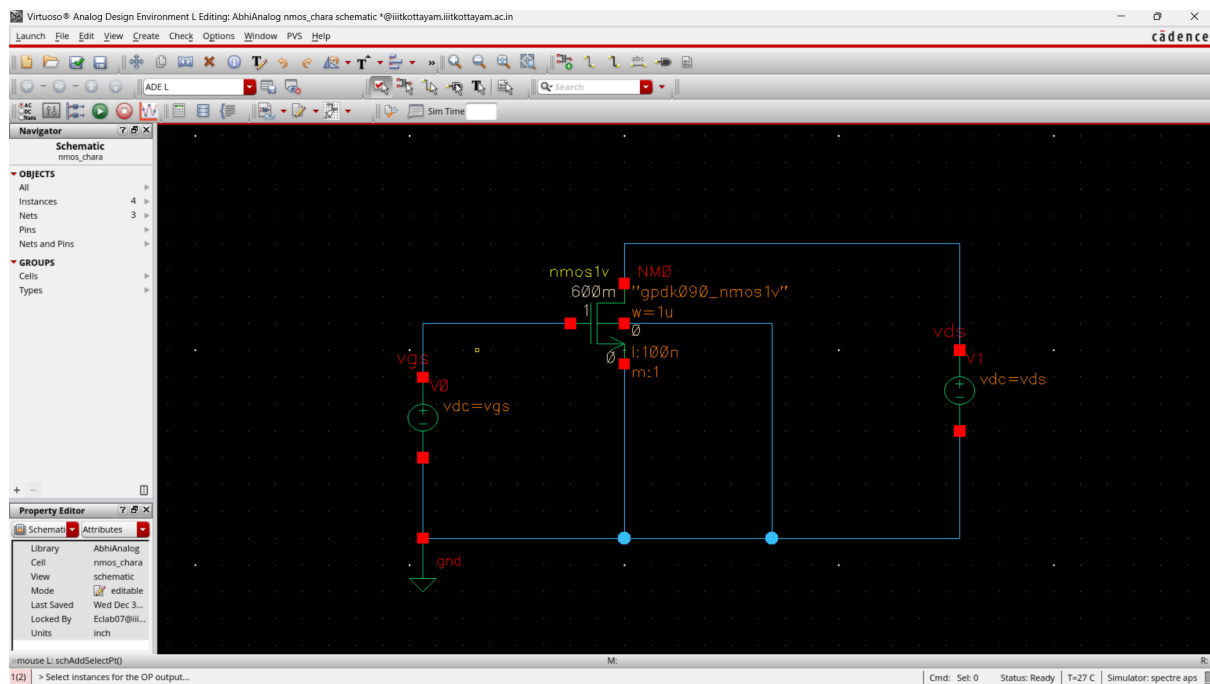


NMOS Characterization

Github repo link:

https://github.com/Abhiram-Jayakumar-07/AnalogElectronicsLab_2025BEC0020/tree/main/NMOS%20Characterization


Schematic:




Results:

region	2
reversed	0
ron	1.027K
rout	3.4383K
sdint	2.14748G
sdop	-1
self_gain	3.12136
tau1	NaN
tk	NaN
trise	NaN
ueff	16.7749m
vbs	0
vdb	600m
vds	600m
vdsat	402.099m
vdsat_marg	NaN
vdss	402.099m
vearly	2.00873
vfbeff	-899.062m
vgb	1
vgd	400m
vgs	1
vgsteff	770.042m
vgt	788.53m
vsat_marg	197.901m
vsb	-0
vth	211.47m
vth0	NaN
vth_drive	NaN

I_D vs V_{GS} DC Analysis Graph:

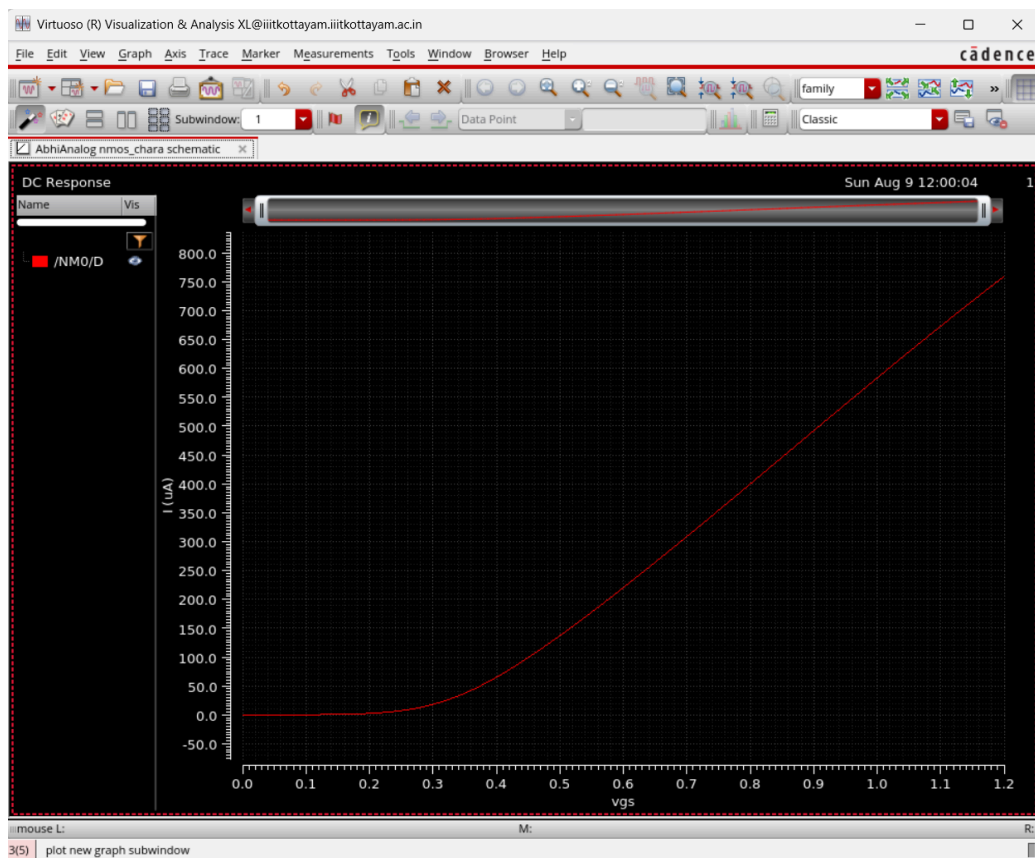

I_D vs V_{DS} DC Analysis Graph:

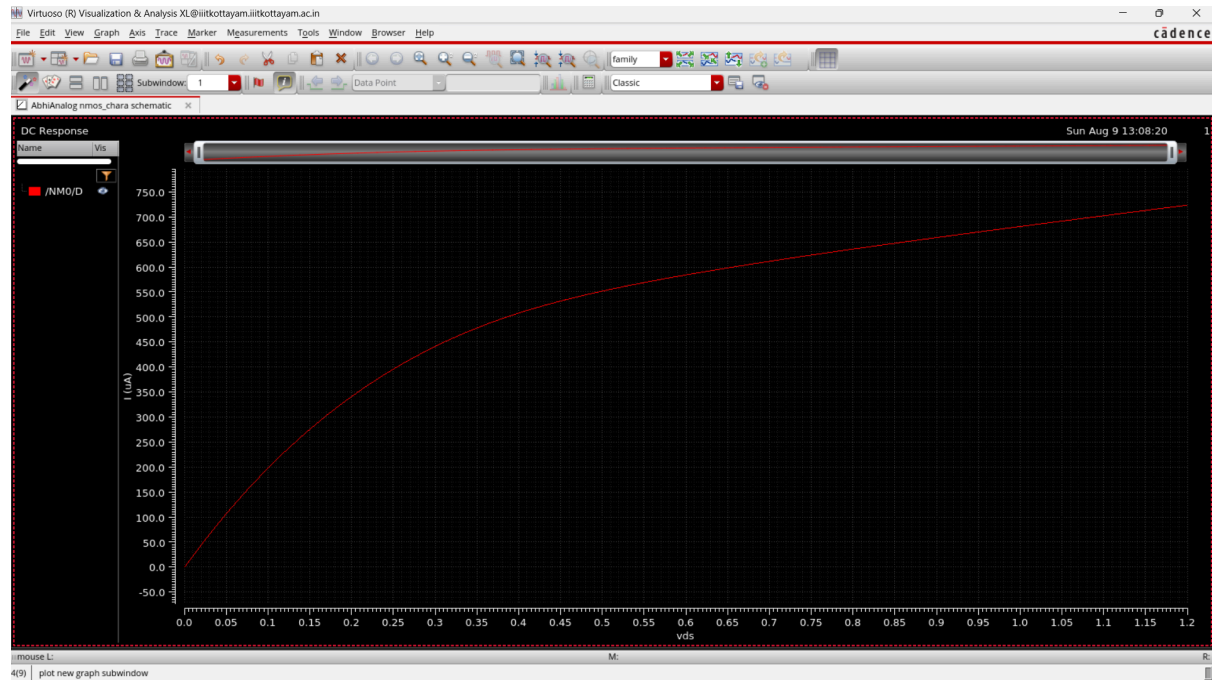

I_D vs V_{DS} Parametric Analysis Graph:

